

Simple Circuits

Resistor \underbrace{R}_{V} $I \rightarrow$ current $R \equiv$ resistance
Ohm's Law: $V = IR$

Capacitor \underbrace{C}_{V} $I \rightarrow$ charge $Q = CV \Rightarrow I = C \frac{dV}{dt}$

Inductor \underbrace{L}_{V} $I \rightarrow$ $V = L \frac{dI}{dt}$

Impedance + Reactance

Voltages and currents as complex numbers:

$$V(t) = V_0 \cos(\omega t + \phi) \equiv \text{Re} \left[e^{i\omega t} V_0 e^{i\phi} = (a + ib) e^{i\omega t} \right]$$

Reactance: \rightarrow $I(t) = \text{Re} \left[V_0 e^{i\omega t} / (-i/\omega C) \right] = \text{Re} \frac{V_0 e^{i\omega t}}{X_C}$
 $X_C = -\frac{i}{\omega C}$

\lll $X_L = i\omega L$

Impedance (generalized Ohm's law):

$$\underline{Z} \quad V = I Z$$

Series elements: $Z = \sum_n Z_n$
Parallel elements: $Z^{-1} = \sum_n Z_n^{-1}$

$$Z_R = R \quad Z_C = -\frac{i}{\omega C} \quad Z_L = i\omega L$$

Transfer function of a network

$$X(\omega) \begin{array}{c} \circ \\ \circ \end{array} \boxed{g(\omega)} \begin{array}{c} \circ \\ \circ \end{array} Y(\omega) = g(\omega) X(\omega)$$

$g(\omega)$ is complex: $g_0 e^{i\phi}$ $\phi = \text{phase shift}$

If $X(\omega) = X_0 e^{i\omega t}$, $Y(\omega) = X_0 g_0 e^{i(\omega t + \phi)}$

In time domain $X(t) = \frac{1}{2\pi} \int X(\omega) e^{-i\omega t} d\omega$

$$Y(t) = \frac{1}{2\pi} \int g(\omega) X(\omega) e^{-i\omega t} d\omega$$


$$Y(t) = \widetilde{g(\omega)} * \widetilde{X(\omega)} = g(t) \cdot X(t)$$

where $g(t) = \frac{1}{2\pi} \int e^{-i\omega t} g(\omega) d\omega$

Example 1: To measure $g(t)$ apply pulse $X(t) = \delta(t)$
 \rightarrow output $Y(t) = g(t)$

Example 2: For broadband amplifier $g(\omega) = \text{constant}$.
 $Y(t) \sim X(t) \rightarrow$ no distortion

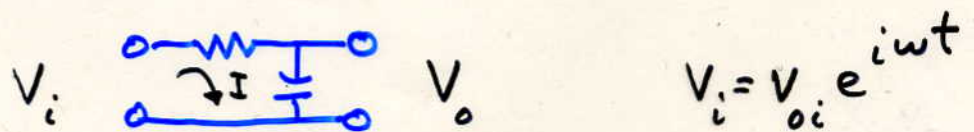Example 3: Choose single pole low-pass filter for $g(\omega)$



$$I = V_i / Z = V_i / \left(\frac{1}{i\omega C} + R \right)$$

$$V_i = V_{oi} e^{i\omega t}$$

$$V_o = I / i\omega C$$

$$g = \frac{V_o}{V_i} = \frac{1}{1 + i\omega RC} = \frac{1 - i\omega RC}{1 + \omega^2 R^2 C^2}$$

note $\tan \phi = \omega RC$
time constant $\tau = RC$

$$|g| = \left| \frac{V_o}{V_i} \right| = \frac{1}{(1 + \omega^2 R^2 C^2)^{1/2}}$$


For $\omega\tau \gg 1$ $|g| \sim \omega^{-1}$ Power $\sim \omega^{-2}$

For each factor of 2 in frequency [octave]
power decreases $\times \frac{1}{4}$

Define dB = $10 \log_{10}$

$\therefore 10 \log_{10}(\frac{1}{4}) = 6 \text{ dB / Octave "roll off"}$

Effective Bandwidth

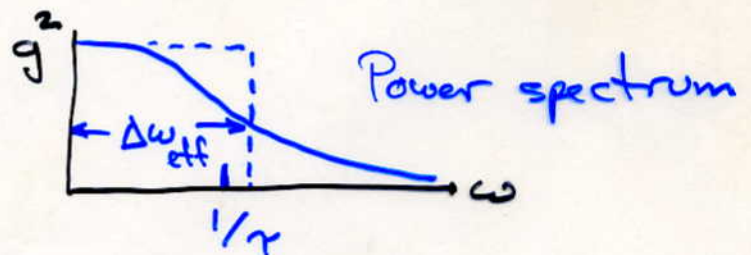


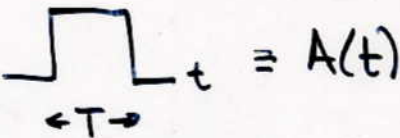
$$\Delta\omega_{\text{eff}} = \frac{\int_0^{\infty} |g(\omega)|^2 d\omega}{|g(0)|^2}$$

$$= \frac{1}{\tau} \int_0^{\infty} \frac{d(\omega\tau)}{1 + \omega^2\tau^2} = \frac{\pi}{2\tau}$$

$$\Rightarrow \Delta f_{\text{eff}} = \frac{1}{4\tau} = \frac{1}{4RC}$$

Example 4: Running average
(usually implemented digitally)

Given time stream $x(t)$ 

convolve with  $\equiv A(t)$

$x(t) * A(t) \equiv g(\omega) \cdot X(\omega)$ where


gain $g(\omega) = \frac{2}{\omega T} \sin\left(\frac{\omega T}{2}\right)$ sinc function

$$\text{then } \Delta\omega_{\text{eff}} = \frac{2}{T} \int_0^{\infty} \left(\frac{2}{\omega T}\right)^2 \sin^2\left(\frac{\omega T}{2}\right) d\left(\frac{\omega T}{2}\right) = \frac{\pi}{T}$$

$$\therefore \Delta f_{\text{eff}} = \frac{1}{2T}$$

Useful properties of Power Spectrum

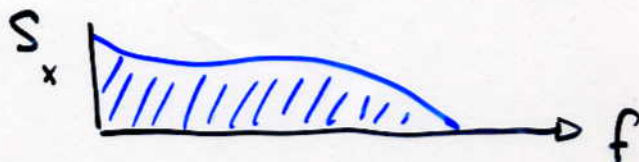Variance of $X(t) = \langle (X - \bar{X})^2 \rangle = \overline{X^2} = \int_0^{\infty} S_x(f) df$
(for stationary process), $\bar{X} = 0$




$$\overline{X^2} = \text{area under } S_x(f)$$

Apply a noise signal $x(t)$ with power spectrum $S_x(f)$ to a circuit with complex gain $g(f)$.

$$\text{Variance of output is } \overline{Y^2} = \int_0^{\infty} S_x(f) |g(f)|^2 df$$

In special case where $|g(f)|^2$ has a relatively narrow peak compared with structure in $S_x(f)$

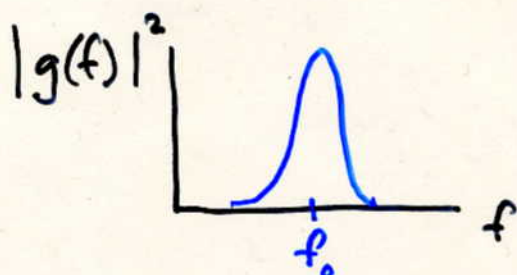

$$\overline{Y^2} = S_x(f_0) \int_0^{\infty} |g(f)|^2 df = S_x(f_0) |g(f_0)|^2 \Delta f_{\text{eff}}$$

This is the basis of effective bandwidth

$$B_{\text{eff}} = \Delta f_{\text{eff}} = \int_0^{\infty} \frac{|g(f)|^2}{|g(f_0)|^2} df$$

\Rightarrow In practice, a narrow band filter can be used to measure $S_x(f)$

